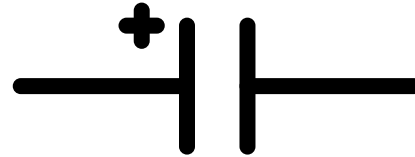


# Electronic Components, Basic Circuits

# An Introduction to Circuits

- ◎ Basic Electronic Components
  - > Capacitors
  - > Resistors
  - > Diodes
  - > Switches
  - > Power supplies

# Capacitors



- ◎ What are They?
  - > Parallel conductive plates separated by an insulator
- ◎ Uses in Circuits
  - > Store and disperse charge (denouncing circuits)
- ◎ Types of Capacitors
  - > Fixed-capacitance
  - > Variable capacitance
- ◎ Connections
  - > Dedicated + and – terminals (2 leads)

# Resistors



- ◎ What are They?
  - > High-resistive metal alloy surrounded by a carbon casing
- ◎ Uses in Circuits
  - > Limit voltage and current
- ◎ Types of Resistors
  - > Fixed-resistance
  - > Rheostat
  - > Potentiometer
- ◎ Connections
  - > 2 terminals (voltage independent), 3 terminals (+, –, and signal)

# Resistors (cont.)

## Reading Resistor Color Codes


- > 4 and 5 color band resistors
- > Resistance measured in ohms ( $\Omega$ )
- > Last band measures tolerance (%)

COLOR	1st BAND	2nd BAND	3rd BAND	MULTIPLIER	TOLERANCE
Black	0	0	0	1 $\Omega$	
Brown	1	1	1	10 $\Omega$	$\pm 1\%$ (F)
Red	2	2	2	100 $\Omega$	$\pm 2\%$ (G)
Orange	3	3	3	1K $\Omega$	
Yellow	4	4	4	10K $\Omega$	
Green	5	5	5	100K $\Omega$	$\pm 0.5\%$ (D)
Blue	6	6	6	1M $\Omega$	$\pm 0.25\%$ (C)
Violet	7	7	7	10M $\Omega$	$\pm 0.10\%$ (B)
Grey	8	8	8		$\pm 0.05\%$
White	9	9	9		
Gold				0.1	$\pm 5\%$ (J)
Silver				0.01	$\pm 10\%$ (K)

Electronix Express / RSR  
<http://www.elexp.com>

1-800-972-2225  
 In NJ 732-381-8020

# Diodes

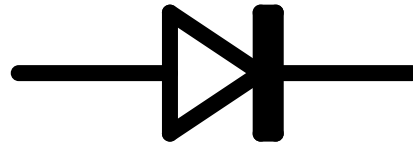


- ◎ What are They?
  - > Insulated p-type and n-type silicon plates
- ◎ Uses in Circuits
  - > Allow the flow of current only in one direction
- ◎ Types of Diodes
  - > LEDs (Light Emitting Diodes)
  - > Zener/Schottky diodes (voltage regulation)
- ◎ Connections
  - > Dedicated + and – terminals (2 or 3 leads)

# Switches



- ◎ What are They?
  - > Breakable connections within a circuit
- ◎ Uses in Circuits
  - > Opens or closes a circuit, switches connections
- ◎ Types of Switches
  - > ON/OFF
  - > ON/OFF/ON
- ◎ Connections
  - > Varies (usually 2 or 3 terminals, no dedicated leads)


# Transistors

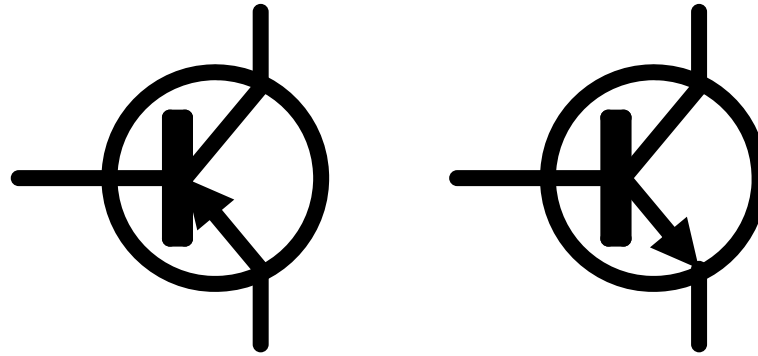

- ◎ What are They?
  - > Solid-state silicon switch
- ◎ Uses in Circuits
  - > Switches or amplifies electronic signals
- ◎ Types of Transistors
  - > PNP
  - > NPN
- ◎ Connections
  - > Dedicated terminals for base, collector, and emitter pins (BCE)



# Power Supplies

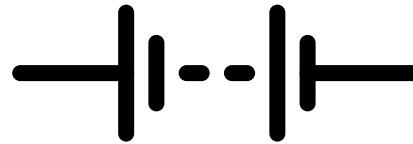

- ◎ What are They?
  - > Power cells or batteries
- ◎ Uses in Circuits
  - > Create voltage to drive circuits
- ◎ Types of Power Supplies
  - > Single power cell
  - > Battery
- ◎ Connections
  - > Dedicated terminals for + and – leads

# An Introduction to Circuits

- ◎ Network Capacitors and Resistors
  - > Capacitors in series and parallel configuration
  - > Resistors in series and parallel configuration



# Capacitors in Series and Parallel

## Series Configuration

- > Current remains constant; voltage does not
- > Net capacitance:  $1/C_1 + 1/C_2 + \dots + 1/C_n = 1/C_c$
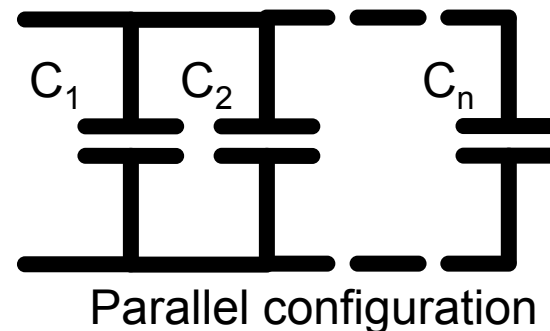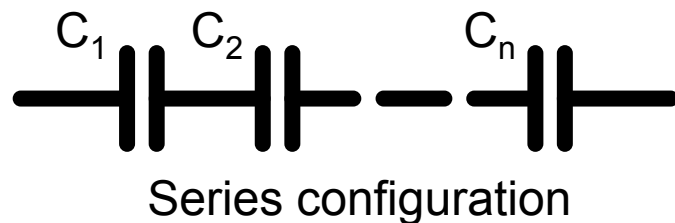
## Parallel Configuration

- > Voltage remains constant; current does not
- > Net capacitance:  $C_1 + C_2 + \dots + C_n = C_c$



# Resistors in Series and Parallel

## Series Configuration


- > Current remains constant; voltage does not
- > Net resistance:  $R_1 + R_2 + \dots + R_n = R_r$

## Parallel Configuration

- > Voltage remains constant; current does not
- > Net resistance:  $1/R_1 + 1/R_2 + \dots + 1/R_n = 1/R_r$



Series configuration

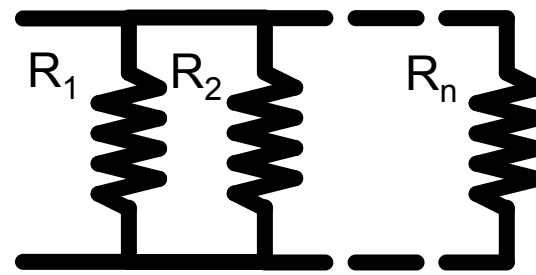

Parallel configuration

# An Introduction to Circuits

- ◎ Laws of Circuits
  - > Ohm's Law
  - > Watt's Law
  - > Kirchhoff's Law

# Ohm's Law

## Description


- > Relates the difference in potential (voltage) of a circuit as a function of the current and the resistance of the circuit

## Formula

- >  $V = I \cdot R$
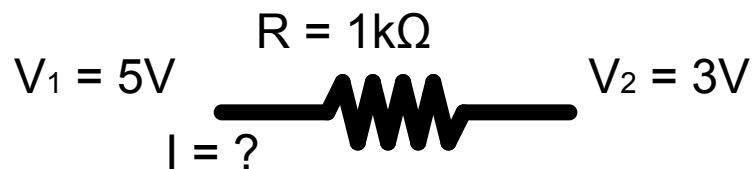
## Example

- >  $(V_1 - V_2) = I \cdot R$
- >  $(5V - 3V) = I \cdot (1000\Omega)$
- >  $I = 2V/1000\Omega = 0.002A$



# Watt's Law

- ◎ Description

- > Relates the power of a circuit as a function of the voltage and current of the circuit

- ◎ Formula


- >  $P = V \cdot I = I^2 R$

- ◎ Example

- >  $P = (V_1 - V_2) \cdot I$


- >  $P = (5V - 3V) \cdot (0.010A)$

- >  $P = 0.02W$

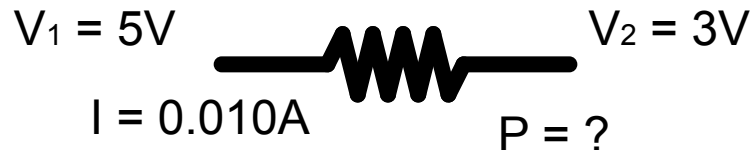
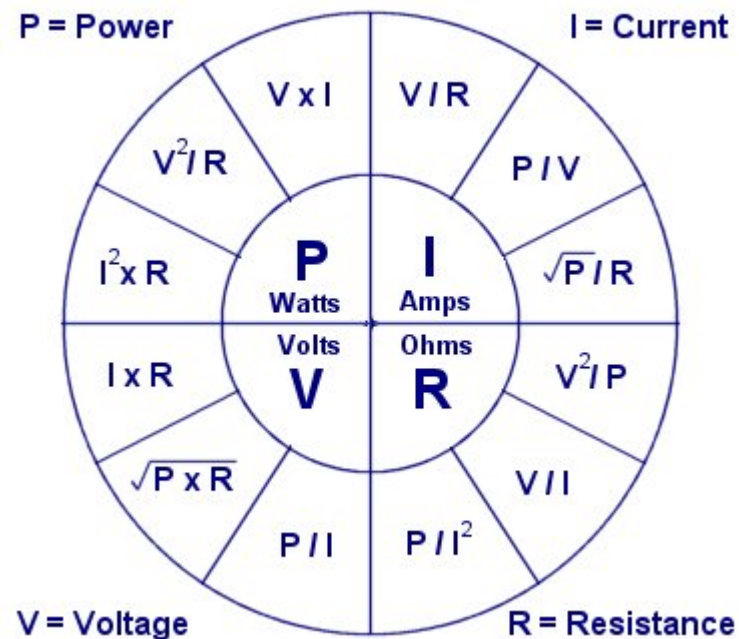
# Watt's Law (cont.)

- Relationship of Voltage, Current, and Resistance





# Kirchhoff's Law

## ⊙ Descriptions

- > Indicates that the sum of the potential differences through the circuit must be zero (Voltage Law)
- > Indicates that the sum of the currents from a wire branch must be equal to the input current (Current Law)

## ⊙ Formulas

- >  $\sum V = 0$
- >  $I_s = I_1 + I_2 + \dots + I_n$

# Kirchhoff's Law (cont.)

## Examples

>  $I = V/R$


>  $R_r = R_1 + R_2$

>  $R_r = 12\text{k}\Omega$

>  $I = (5\text{V} - 0\text{V})/12\text{k}\Omega = 4.167 \cdot 10^{-4}\text{A}$

>  $V_a = 5\text{V} - I \cdot R_1$

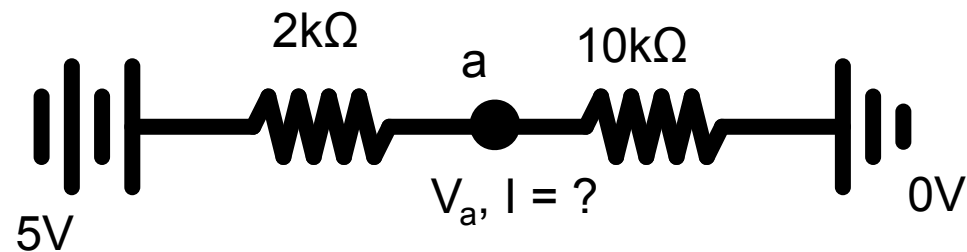
>  $V_a = 5\text{V} - (4.167 \cdot 10^{-4}\text{A}) \cdot 2\text{k}\Omega = 4.167\text{V}$



# Kirchhoff's Law (cont.)
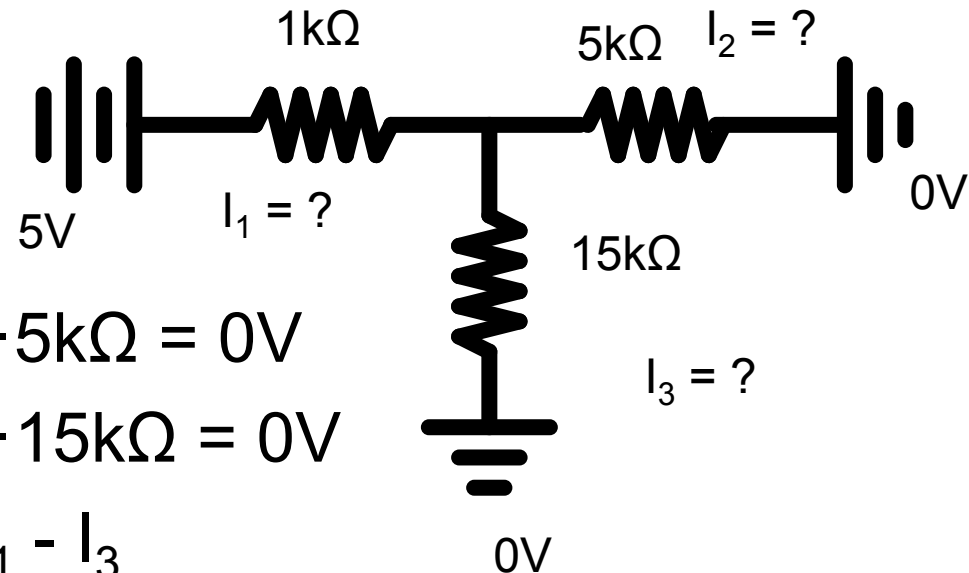
## Examples

- >  $\Sigma V = 0$
- >  $5V - I_1 \cdot 1k\Omega - I_2 \cdot 5k\Omega = 0V$
- >  $5V - I_1 \cdot 1k\Omega - I_3 \cdot 15k\Omega = 0V$
- >  $I_1 = I_2 + I_3, I_2 = I_1 - I_3$
- > 3 linear equations, 3 variables
- >  $I_1 = 1.053 \text{ mA}$
- >  $I_2 = 0.789 \text{ mA}$
- >  $I_3 = 0.264 \text{ mA}$



# Additional Resources

- ◎ Wikipedia

- > <http://www.wikipedia.org/>

- ◎ Circuit Info

- > <http://www.kpsec.freeuk.com/index.htm>